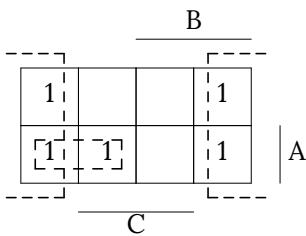


Homework on simplifying expressions using Karnaugh Maps and designing circuits using NAND and NOR gates from them

Sudipto Mallick
(Serial No.: 571)

1. $f = \Sigma(0, 2, 4, 5, 6)$

The K-Map for this boolean expression of 3 variables is




The simplified form is


$$f = A\bar{B} + \bar{C}$$

The expression suitable to form a circuit using NAND gate is
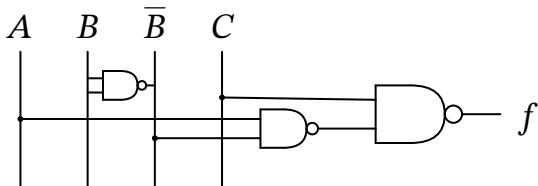
$$\begin{aligned} f = \bar{\bar{f}} &= \overline{A\bar{B} + \bar{C}} \\ &= \overline{A\bar{B}} \cdot \overline{\bar{C}} \\ &= \overline{A \cdot B} \cdot C \\ &= A \cdot B \cdot C \end{aligned}$$



The K-map for \bar{f} is

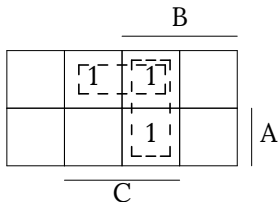

The simplified expression for \bar{f} is


$$\bar{f} = \bar{A}C + BC$$

The expression suitable to implement the given expression using NOR gates is calculated as follows:

$$\bar{\bar{f}} = \overline{\bar{A}C + BC}$$


$$f = \overline{\bar{A}C} \cdot \overline{BC}$$
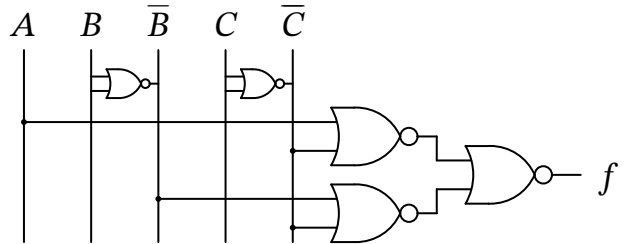
$$\begin{aligned} f = \bar{\bar{f}} &= \overline{\bar{A}C} \cdot \overline{BC} \\ &= \overline{\bar{A}C} + \overline{BC} \\ &= \overline{\bar{A} \cdot C} + \overline{B \cdot C} \\ &= \overline{\bar{A}} + \overline{C} + \overline{B} + \overline{C} \end{aligned}$$



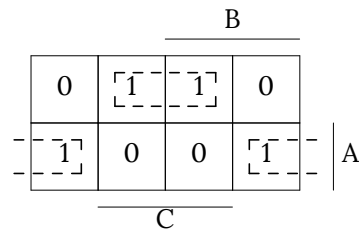2. $f = \Pi(0, 2, 5, 7)$

The K-Map for this boolean expression of 3 variables is




The simplified form is


$$f = \bar{A}C + A\bar{C}$$

The expression suitable to form a circuit using NAND gate is
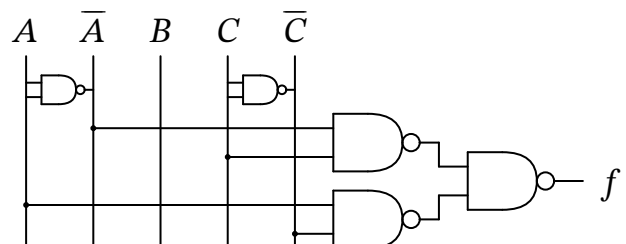
$$\begin{aligned} f = \bar{\bar{f}} &= \overline{\bar{A}C + A\bar{C}} \\ &= \overline{\bar{A} \cdot C} \cdot \overline{A \cdot \bar{C}} \\ &= A \cdot C \cdot A \cdot C \end{aligned}$$



The K-map for \bar{f} is

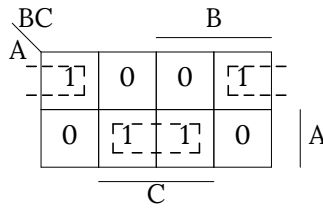

The simplified form of \bar{f} is

$$\bar{f} = \bar{A}\bar{C} + AC$$

The expression suitable to implement the given expression using NOR gates is calculated as follows:

$$\bar{f} = \bar{A}\bar{C} + AC$$

$$f = \overline{\bar{A}\bar{C} \cdot AC}$$


$$f = \bar{f} = \overline{\bar{A}\bar{C} \cdot AC}$$

$$= \overline{\bar{A}\bar{C}} + \overline{AC}$$

$$= \overline{\bar{A} + \bar{C}} + \overline{A + C}$$


$$= \overline{\bar{A} + \bar{C}} + \overline{A + C}$$

A \bar{A} B C \bar{C}

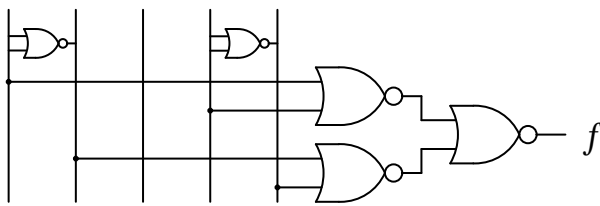

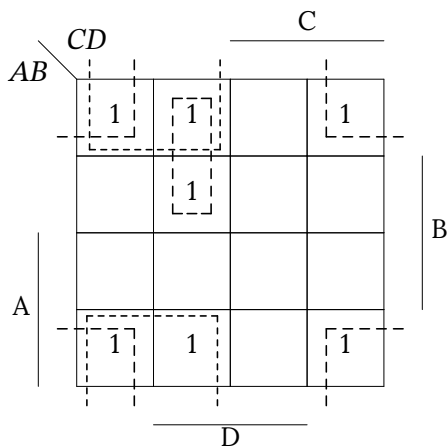3. $f = \sum(0, 1, 2, 5, 8, 9, 10)$

The K-Map of this boolean function of 4 variables is



The simplified form is


$$f = \bar{B}\bar{D} + \bar{B}\bar{C} + \bar{A}\bar{C}D$$

The expression suitable to form a circuit using NAND gate is

$$f = \bar{f} = \overline{\bar{B}\bar{D} + \bar{B}\bar{C} + \bar{A}\bar{C}D}$$

$$= \overline{\bar{B}\bar{D}} \cdot \overline{\bar{B}\bar{C}} \cdot \overline{\bar{A}\bar{C}D}$$

The K-map for \bar{f} is

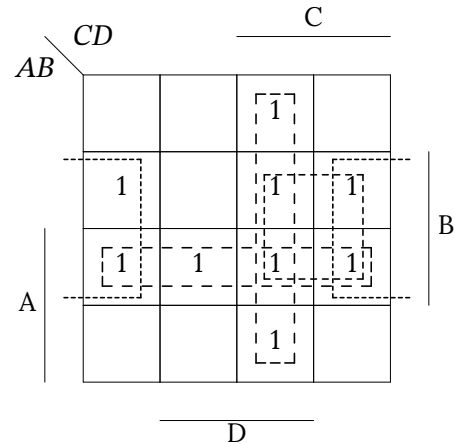

The simplified expression for \bar{f} is

$$\bar{f} = AB + BC + CD + B\bar{D}$$

The expression suitable to implement the given expression using NOR gates is calculated as follows:

$$\bar{f} = AB + BC + CD + B\bar{D}$$

$$f = \overline{\bar{A}\bar{B} \cdot \bar{B}\bar{C} \cdot \bar{C}\bar{D} \cdot \bar{B}\bar{D}}$$

$$f = \bar{f} = \overline{\bar{A}\bar{B} \cdot \bar{B}\bar{C} \cdot \bar{C}\bar{D} \cdot \bar{B}\bar{D}}$$

$$= \overline{\bar{A}\bar{B}} + \overline{\bar{B}\bar{C}} + \overline{\bar{C}\bar{D}} + \overline{\bar{B}\bar{D}}$$

$$= \overline{\bar{A} + \bar{B}} + \overline{\bar{B} + \bar{C}} + \overline{\bar{C} + \bar{D}} + \overline{\bar{B} + \bar{D}}$$

Figure: The boolean function $\Sigma(0, 1, 2, 5, 8, 9, 10)$ implemented using NAND gates

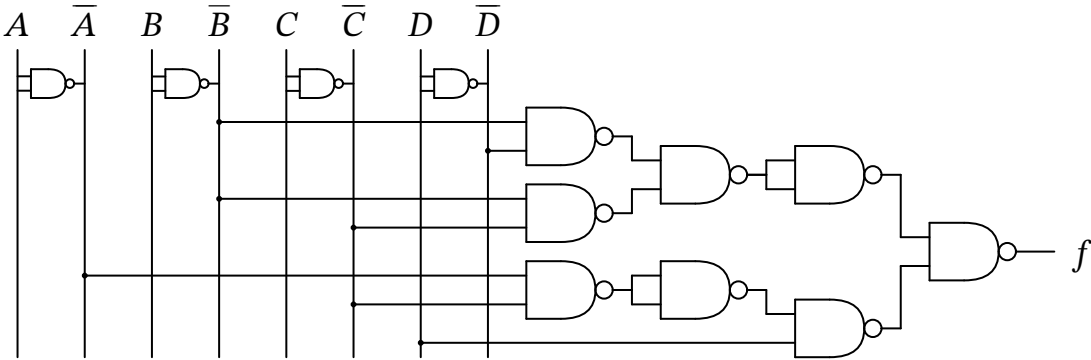


Figure: The boolean function $\Sigma(0, 1, 2, 5, 8, 9, 10)$ implemented using NOR gates

